

• Chapter 2:

2.1, 2.4, 2.16, 2.25, 2.32, 2.40,  
2.67, 2.71, 2.77, 2.83, 2.85, 2.97

P2.1\* (a)  $R_{eq} = 20 \Omega$  (b)  $R_{eq} = 23 \Omega$


P2.4\* The  $12\text{-}\Omega$  and  $6\text{-}\Omega$  resistances are in parallel having an equivalent resistance of  $4 \Omega$ . Similarly, the  $18\text{-}\Omega$  and  $9\text{-}\Omega$  resistances are in parallel and have an equivalent resistance of  $6 \Omega$ . Finally, the two parallel combinations are in series, and we have

$$R_{ab} = 4 + 6 = 10 \Omega$$

P2.16  $R = 10 \Omega$ .

P2.25\* Combining resistors in series and parallel, we find that the equivalent resistance seen by the current source is  $R_{eq} = 17.5 \Omega$ .

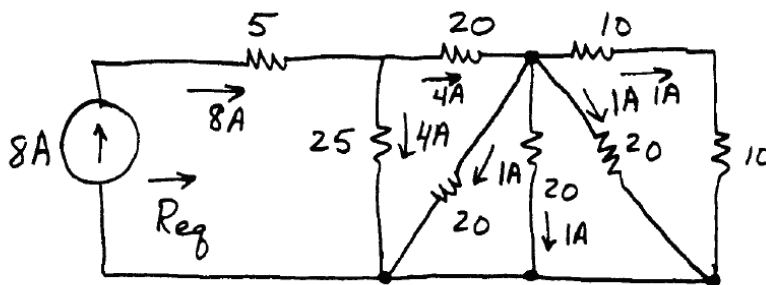Thus,  $v = 8 \times 17.5 = 140 \text{ V}$ . Also,  $i = 1 \text{ A}$ .




P2.32 With the switch open, the current flowing clockwise in the circuit is given by  $i = \frac{16}{6 + R_2}$ , and we have  $v_2 = R_2 i = \frac{16R_2}{6 + R_2} = 10$ . Solving, we find  $R_2 = 10 \Omega$ .

With the switch closed,  $R_2$  and  $R_L$  are in parallel with an equivalent resistance given by  $R_{eq} = \frac{1}{1/R_2 + 1/R_L} = \frac{1}{1/10 + 1/R_L}$ . The current through  $R_{eq}$  is given by  $i = \frac{16}{6 + R_{eq}}$  and we have  $v_2 = R_{eq}i = \frac{16R_{eq}}{6 + R_{eq}} = 8$ . Solving, we find  $R_{eq} = 6 \Omega$ . Then, we can write  $R_{eq} = \frac{1}{1/10 + 1/R_L} = 6$ . Solving, we find  $R_L = 15 \Omega$ .

P2.40 (a)  $R_1 + R_2 = \frac{9V}{10mA} = 900 \Omega$        $\frac{R_2}{R_1 + R_2} \times 9 = 5$

Solving, we find  $R_2 = 500 \Omega$  and  $R_1 = 400 \Omega$ .

(b)

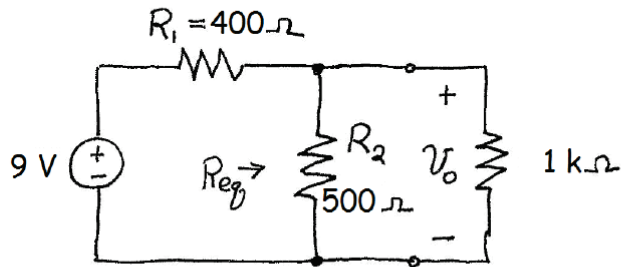

The equivalent resistance for the parallel combination of  $R_2$  and the load is

$$R_{eq} = \frac{1}{1/500 + 1/1000} = 333.3 \Omega$$

Then, using the voltage division principle, we have

$$v_o = \frac{R_{eq}}{R_1 + R_{eq}} \times 9V = 4.091V$$

(c) If we choose a larger current in part (a), resulting in smaller values for  $R_1$  and  $R_2$ , the loaded voltage in part (b) would be closer to 5 V. However, this would result in shorter battery life.

**P2.67\*** Writing KVL equations around each mesh, we have

$$5i_1 + 15(i_1 - i_2) = 20 \quad \text{and} \quad 15(i_2 - i_1) + 10i_2 = 10$$

Putting the equations into standard form we have

$$20i_1 - 15i_2 = 20 \quad \text{and} \quad -15i_1 + 25i_2 = 10$$


Solving, we obtain  $i_1 = 2.364$  A and  $i_2 = 1.818$  A.

Then, the power delivered to the  $15\text{-}\Omega$  resistor is  $P = (i_1 - i_2)^2 15 = 4.471$  W.

**P2.71** Writing and simplifying the mesh equations, we obtain:

$$40i_1 - 20i_2 = 10$$


$$-20i_1 + 40i_2 = 0$$

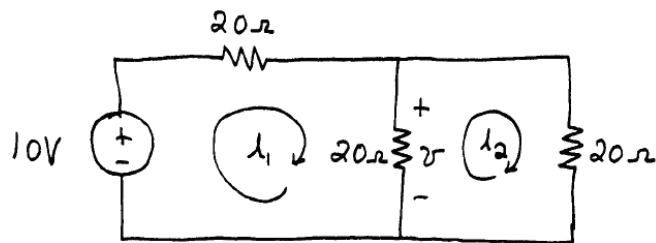

Solving, we find  $i_1 = 0.3333$  and  $i_2 = 0.1667$ .

Thus,  $v = 20(i_1 - i_2) = 3.333$  V.

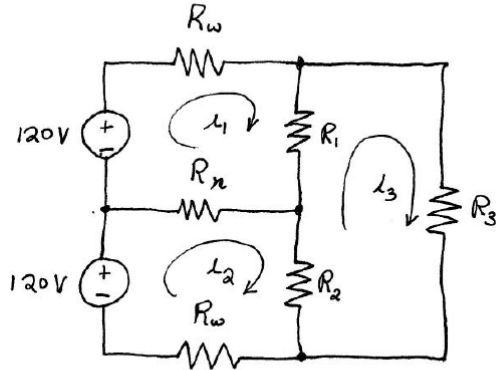P2.77 (a) First, we select mesh-current variables as shown.



Then, we can write

$$(R_w + R_n + R_1)i_1 - R_n i_2 - R_1 i_3 = 120$$

$$-R_n i_1 + (R_w + R_n + R_2)i_2 - R_2 i_3 = 120$$

$$-R_1 i_1 - R_2 i_2 + (R_1 + R_2 + R_3)i_3 = 0$$

Alternatively, because the network consists of independent voltage sources and resistances, and all of the mesh currents flow clockwise, we can enter the matrices directly into MATLAB.

```
Rw = 0.1; Rn=0.1; R1 = 20; R2 = 10; R3 = 16;
```

```
R = [Rw+Rn+R1 -Rn -R1; -Rn Rw+Rn+R2 -R2; -R1 -R2 R1+R2+R3];
```

```
V = [120; 120; 0];
```

```
I = R\V;
```

```
% Finally, we compute the voltages across the loads.
```

```
Vr1 = R1*(I(1) - I(3)), Vr2 = R2*(I(2) - I(3)), Vr3 = R3*I(3)...
```

```
% which results in:
```

```
Vr1 =
```

```
118.5121
```

```
Vr2 =
```

```
116.7862
```

```
Vr3 =
```

```
235.2983
```


These values are within the normal range for nearly all devices.

(b) Next, we change  $R_n$  to a very high value such as  $10^9$  which for practical calculations is equivalent to an open circuit, and again compute the voltages resulting in:

$$\begin{aligned} V_{r1} &= \\ &156.9910 \\ V_{r2} &= \\ &78.4955 \\ V_{r3} &= \\ &235.4865 \end{aligned}$$

The voltage across  $R_1$  is certainly high enough to damage most loads designed to operate at 110 to 120 V.

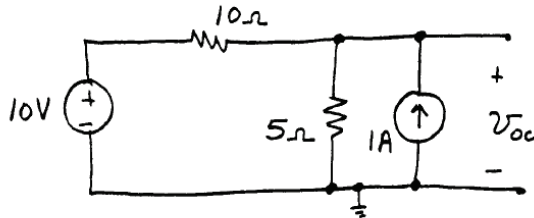
**P2.83\*** First, we write a node voltage equation to solve for the open-circuit voltage:





$$\frac{v_{oc} - 10}{10} + \frac{v_{oc}}{5} = 1$$

Solving, we find  $v_{oc} = 6.667$  V.

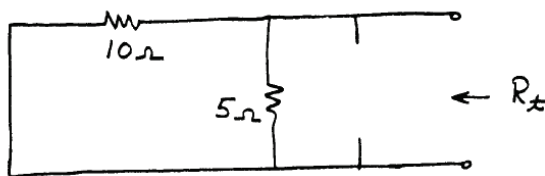
Then zeroing the sources, we have this circuit:



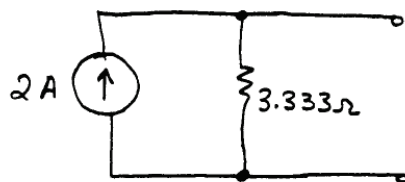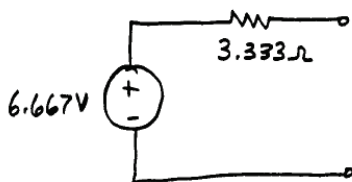
Thus,  $R_t = \frac{1}{1/10 + 1/5} = 3.333 \Omega$ . The Thévenin and Norton equivalents are:



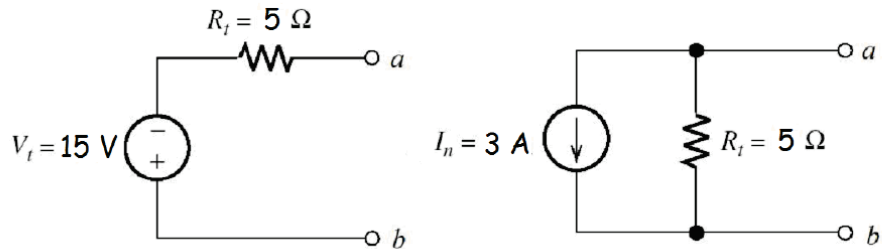- P2.85** The  $9\text{-}\Omega$  resistor has no effect on the equivalent circuits because the voltage across the  $12\text{-V}$  source is independent of the resistor value.




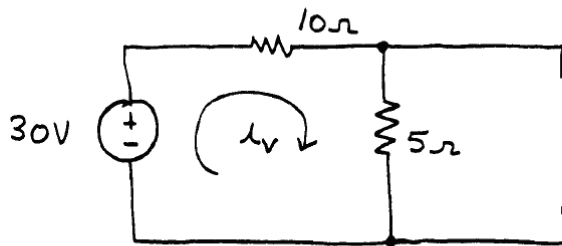- P2.97\*** First, we zero the current source and find the current due to the voltage source.



$$i_v = 30/15 = 2 \text{ A}$$

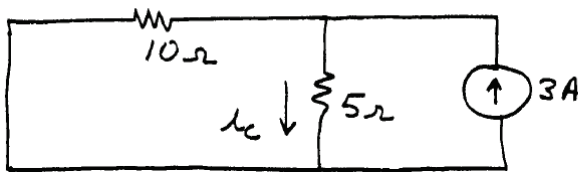Then, we zero the voltage source and use the current-division principle to find the current due to the current source.



$$i_c = 3 \frac{10}{5+10} = 2 \text{ A}$$

Finally, the total current is the sum of the contributions from each source.

$$i = i_v + i_c = 4 \text{ A}$$