

**P2.57\***

$$v_x = v_2 - v_1$$

Writing KCL at nodes 1 and 2:

$$\frac{v_1}{5} + \frac{v_1 - 2v_x}{15} + \frac{v_1 - v_2}{10} = 1$$

$$\frac{v_2}{5} + \frac{v_2 - 2v_x}{10} + \frac{v_2 - v_1}{10} = 2$$

Substituting and simplifying, we have

$$15v_1 - 7v_2 = 30 \quad \text{and} \quad v_1 + 2v_2 = 20.$$

Solving, we find  $v_1 = 5.405$  and  $v_2 = 7.297$ .

**P2.59** First, we can write:

$$i_x = \frac{5i_x - v_2}{10}$$

Simplifying, we find  $i_x = -0.2v_2$ .

Then write KCL at nodes 1 and 2:


$$\frac{v_1 - 5i_x}{5} = 3 \qquad \frac{v_2}{10} - i_x = -1$$

Substituting for  $i_x$  and simplifying, we have

$$v_1 - v_2 = 15 \quad \text{and} \quad 0.3v_2 = -3$$

which yield  $v_1 = 25 \text{ V}$  and  $v_2 = -10 \text{ V}$ .


P2.88 Open-circuit conditions:

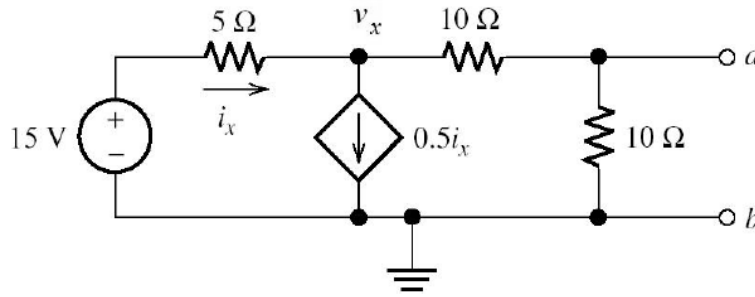

$$i_x = \frac{15 - v_x}{5} \quad \frac{v_x}{10 + 10} - i_x + 0.5i_x = 0 \quad \text{Solving, we find } v_x = 10 \text{ V and}$$


then we have  $V_t = v_{oc} = v_x \frac{10}{10 + 10} = 5 \text{ V}.$

Short-circuit conditions:

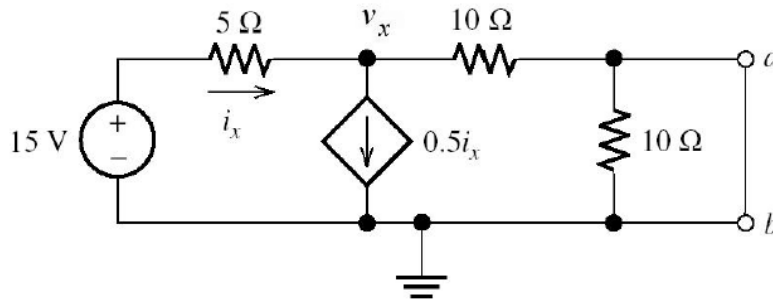


$$i_x = \frac{15 - v_x}{5} \quad \frac{v_x}{10} - i_x + 0.5i_x = 0 \quad \text{Solving, we find } v_x = 7.5 \text{ V and then}$$

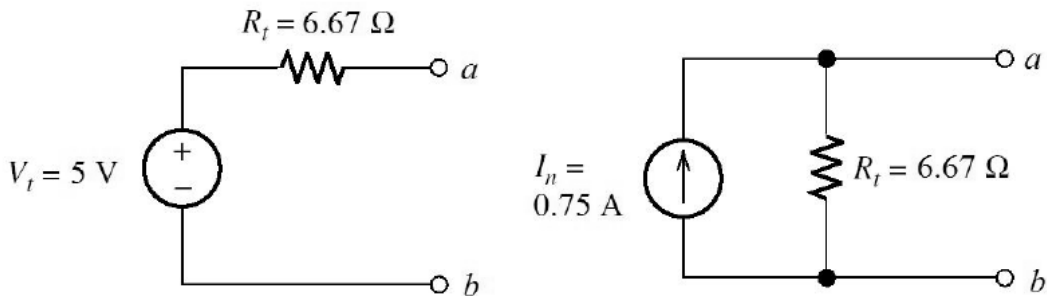
we have  $i_{sc} = \frac{v_x}{10} = 0.75 \text{ A}.$  Then, we have  $R_t = v_{oc} / i_{sc} = 6.67 \Omega.$  Thus the



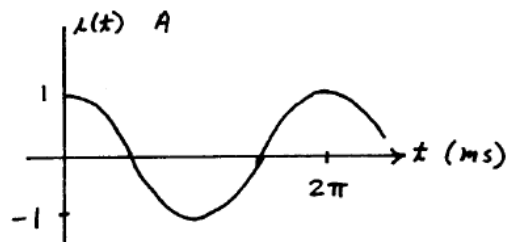P3.6\*  $i(t) = C \frac{dv}{dt} = 10^{-5} \frac{d}{dt}(100 \sin 1000t) = \cos(1000t)$


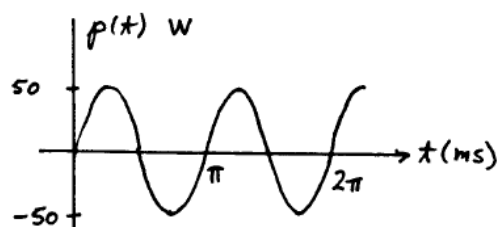
$$p(t) = v(t)i(t) = 100 \cos(1000t) \sin(1000t) = 50 \sin(2000t)$$



$$w(t) = \frac{1}{2} C [v(t)]^2 = 0.05 \sin^2(1000t)$$



P3.7\*

$$v(t) = \frac{1}{C} \int_0^t i(t) dt + v(0)$$

$$v(t) = 2 \times 10^4 \int_0^t 3 \times 10^{-3} dt - 20$$

$$v(t) = 60t - 20 \text{ V}$$

$$p(t) = i(t)v(t) = 3 \times 10^{-3}(60t - 20) \text{ W}$$

Evaluating at  $t = 0$ , we have  $p(0) = -60 \text{ mW}$ . Because the power has a negative value, the capacitor is delivering energy.

At  $t = 1 \text{ s}$ , we have  $p(1) = 120 \text{ mW}$ . Because the power is positive, we know that the capacitor is absorbing energy.

P3.8\*

$$\begin{aligned} W &= \text{power} \times \text{time} = 5 \text{ hp} \times 746 \text{ W / hp} \times 3600 \text{ s} \\ &= 13.4 \times 10^6 \text{ J} \end{aligned}$$

$$V = \sqrt{\frac{2W}{C}} = \sqrt{\frac{2 \times 13.4 \times 10^6}{0.01}} = 51.8 \text{ kV}$$

It turns out that a 0.01-F capacitor rated for this voltage would be much too large and massive for powering an automobile. Besides, to have reasonable performance, an automobile would need much more than 5 hp for an hour.

$$\text{P3.11} \quad Q = Cv = 15 \times 10^{-6} \times 500 = 7.5 \text{ mC}$$

$$W = \frac{1}{2} Cv^2 = \frac{1}{2} \times 15 \times 10^{-6} \times (500)^2 = 1.875 \text{ J}$$

$$P = \frac{\Delta W}{\Delta t} = \frac{1.875}{4 \times 10^{-6}} = 468.75 \text{ kW}$$